

Core short answer questions

Specific instructions to students

- Answer **all** questions in the spaces provided.
- For all questions which require a numerical answer you must show all working.
- You should take the value of g to be 10 ms^{-2} .

A group of students are standing on a bridge, trying to see who can throw a stone the farthest from the bridge, into the river below. Where the students are throwing their stones from is 6.5 m above the water. One of the students measures the time it takes for a stone thrown by someone else to return to the launch height to be 3.6 s.

QUESTION 1 2 marks

What is the initial vertical component of the stone's velocity?

taking up as positive vertically to the top:
 $u = ?$, $v = 0$, $a = -10$,
 $t = 3.60 \div 2 = 1.80$
 $v = u + at$
 $0 = u + -10 \times 1.8$
 $u = 18 \text{ ms}^{-1}$

Answer:

18 ms⁻¹

QUESTION 2 3 marks

What vertical height does the stone reach above the water?


taking up as positive vertically to the top:
 $v = 0$, $a = -10$, $t = 1.8$, $s = ?$
 $s = vt - \frac{1}{2} at^2$
 $= 0 - \frac{1}{2} \times -10 \times 1.8^2$
 $s = 16.2$
 height = $16.2 + 6.5 = 22.7 \text{ m}$

Answer:

22.7 m

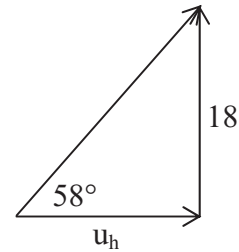QUESTION 3 3 marks

What is the initial horizontal component of the stone's velocity if it leaves the thrower's hand at an angle of 58° to the horizontal?



vertically: $u = 18 \text{ ms}^{-1}$
 $\tan 58^\circ = 18 \div u_h$
 $u_h = 18 \div \tan 58^\circ$
 $= 11.248 \text{ ms}^{-1}$

Answer:

11.2 ms⁻¹

QUESTION 4 4 marks

What horizontal distance from the bridge does the stone travel before it hits the water?

vertically:
 $u = 18$, $a = -10$,
 $s = -6.5$, $t = ?$
 $s = ut + \frac{1}{2} at^2$
 $-6.5 = 18t - 5t^2$
 $5t^2 - 18t - 6.5 = 0$
 solving gives $t = 3.93 \text{ s}$
 horizontally:
 $u = 11.2$, $v = 11.2$,
 $a = 0$, $t = 3.93$, $s = ?$
 $s = ut + \frac{1}{2} at^2$
 $= 11.2 \times 3.93$
 $= 44 \text{ m}$

Answer:

44 m

A 540 g metal ball is rolling along a flat, frictionless surface at a speed of 2.3 ms^{-1} as shown in the diagram.



QUESTION 5 2 marks

How much kinetic energy does the metal ball possess?

$$\begin{aligned} \text{KE} &= \frac{1}{2} mv^2 \\ &= \frac{1}{2} \times 540 \times 10^{-3} \times 2.3^2 \\ &= 1.43 \text{ J or } 1.4 \text{ J} \end{aligned}$$

Answer:

1.4 J

The ball encounters a slope inclined at 32° to the horizontal.

QUESTION 6 2 marks

What vertical height 'h' will the ball reach the slope before it stops and rolls back down?

$$\begin{aligned} \text{KE is converted to GPE} \\ 1.4 &= mgh \\ 1.4 &= 540 \times 10^{-3} \times 10 \times h \\ h &= 0.259 \text{ m} \\ 0.26 \text{ m} \end{aligned}$$

Answer:

0.26 m

The mass of the Moon is $7.35 \times 10^{22} \text{ kg}$ and the mass of the Earth is $5.98 \times 10^{24} \text{ kg}$. The radius of the Moon's orbit around the Earth is $3.84 \times 10^8 \text{ m}$.

QUESTION 7 2 marks

Calculate the magnitude of the gravitational force between the Moon and the Earth.

$$\begin{aligned} F &= G m_{\text{Moon}} m_{\text{Earth}} / r^2 \\ &= (6.67 \times 10^{-11} \times 7.35 \times 10^{22} \times 5.98 \times 10^{24}) \\ &\quad \div (3.84 \times 10^8)^2 \\ &= 1.99 \times 10^{20} \text{ N} \end{aligned}$$

Answer:

$1.99 \times 10^{20} \text{ N}$

QUESTION 8 2 marks

Calculate the magnitude of the Earth's gravitational field at the position of the Moon.

$$\begin{aligned} g &= G m_{\text{Earth}} / r^2 \\ &= (6.67 \times 10^{-11} \times 5.98 \times 10^{24}) \div (3.84 \times 10^8)^2 \\ &= 2.70 \times 10^{-3} \text{ Nkg}^{-1} \end{aligned}$$

Answer:

$2.70 \times 10^{-3} \text{ Nkg}^{-1}$

QUESTION 9 2 marks


Calculate the magnitude of the Moon's gravitational field at the position of the Earth.

$$\begin{aligned} g &= G m_{\text{Moon}} / r^2 \\ &= (6.67 \times 10^{-11} \times 7.35 \times 10^{22}) \div (3.84 \times 10^8)^2 \\ &= 3.32 \times 10^{-5} \text{ Nkg}^{-1} \end{aligned}$$

Answer:

$3.32 \times 10^{-5} \text{ Nkg}^{-1}$

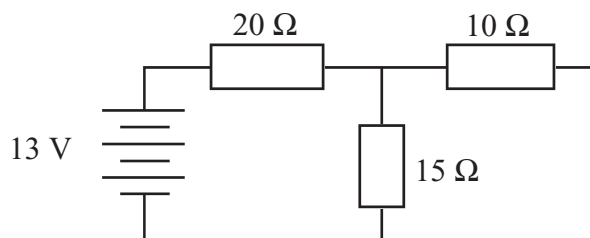Three resistors are connected in a circuit as shown below.



QUESTION 10 2 marks

Calculate the effective resistance of this circuit.

$$\begin{aligned} R_{\text{parallel}} &= (10^{-1} + 15^{-1})^{-1} \\ &= 6 \\ R_{\text{effective}} &= 6 + 20 \\ &= 26 \Omega \end{aligned}$$

Answer:

26 Ω

QUESTION 11 2 marks

Calculate the current flowing through the 20 Ω resistor.

$$\begin{aligned} I &= V \div R \\ &= 13 \div 26 \\ &= 0.5 \text{ A} \end{aligned}$$

Answer:

0.5 A

QUESTION 12

3 marks

Calculate the power output of the $10\ \Omega$ resistor.

$$V_{20} = IR$$

$$= 0.5 \times 20 = 10\ \text{V}$$

$$V_{\text{parallel combination}} = 13 - 10 = 3\ \text{V}$$

$$P_{10} = V^2 \div R$$

$$= 3^2 \div 10$$

$$= 0.9\ \text{W}$$


Answer:

0.9 W

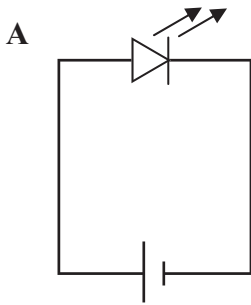
QUESTION 13

2 marks


Which of the following circuit diagrams and bias description is correct for an LED?




forward bias

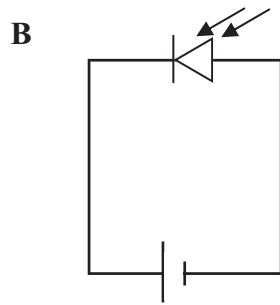

reverse bias

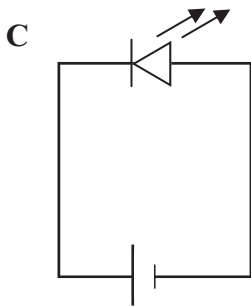

forward bias

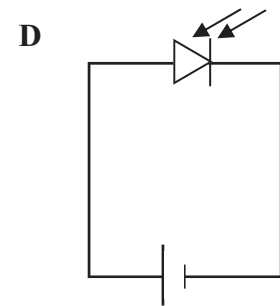

reverse bias

Answer:


A

LEDs operate in forward bias and emit light,


 \therefore the arrows point away from the circuit symbol.**QUESTION 14**

2 marks

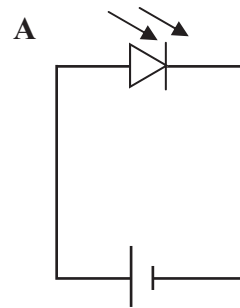
Which of the following circuit diagrams and bias descriptions is correct for a photodiode operating correctly?




forward bias

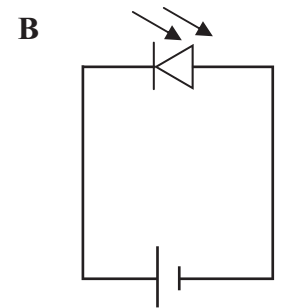

reverse bias

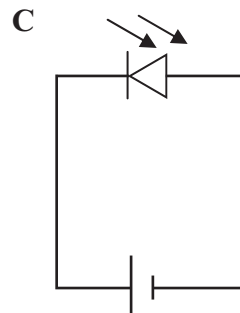

forward bias

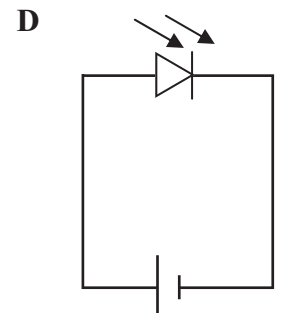

reverse bias

Answer:

B

A photodiode operates correctly when reverse biased


so the symbol 'points' to the left.

An LED is normally connected in a circuit with a limiting resistor and power supply.

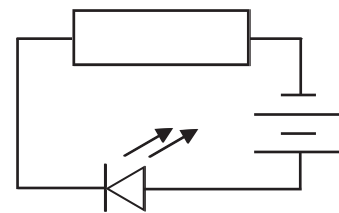QUESTION 15

2 marks

Complete the circuit diagram below to show how such a circuit would be connected.



or similar

QUESTION 16

2 marks

Why is a limiting resistor used in LED circuits?


Answer:

The limiting resistor reduces the potential difference across the LED to the required value and therefore prevents the LED from being damaged.

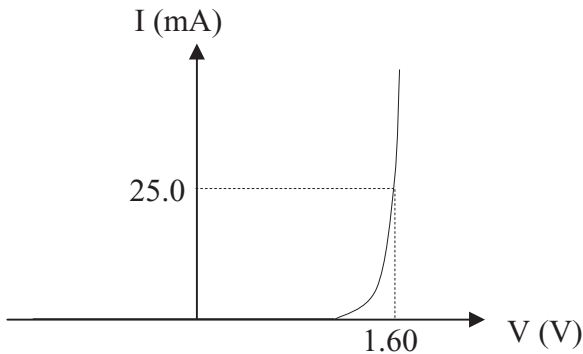QUESTION 17

2 marks

If the graph below represents an I–V characteristic for a typical LED circuit powered by a potential difference of 6 V, what value limiting resistor would be needed?



$$\begin{aligned} V_R &= 6.00 - 1.60 \\ &= 4.40 \text{ V} \\ R &= V \div I \\ &= 4.40 \div (25.0 \times 10^{-3}) \\ &= 176 \Omega \end{aligned}$$

Answer:

176 Ω

In many applications, LEDs are preferable to ordinary light globes.

QUESTION 18

2 marks

What are two advantages of LEDs over ordinary light globes?

Answer:

Any two of the following:

- LEDs are very durable
- LEDs emit light using very low voltages
- LEDs will operate for extended periods of time – up to 500 times longer than ordinary light globes
- LEDs consume much less power than ordinary light globes

An 80 Ω resistor is connected in series with a different LED and a 12 V power supply.

QUESTION 19

3 marks

Calculate the current in mA flowing through the LED if it has a potential difference of 1.8 V across it. Give your answer in mA.

$$\begin{aligned} V_R &= 12 - 1.8 \\ &= 10.2 \text{ V} \\ I &= V \div R = 10.2 \div 80 \\ &= 0.1275 \text{ A} = 128 \text{ mA} \end{aligned}$$

Answer:

128 mA

QUESTION 20

3 marks

This circuit is not ideal to operate the LED. Explain your answer and suggest an alternative arrangement if necessary.

Answer:


The current is quite high and may damage the LED.

A larger resistor would reduce the current to a more suitable level.

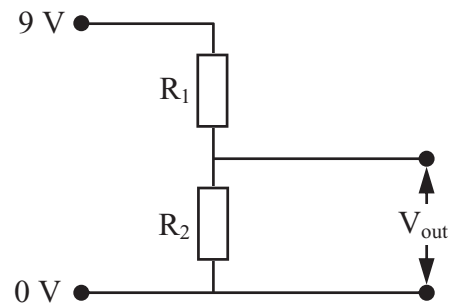QUESTION 21

2 marks

For the voltage divider circuit shown below, what is the output voltage if $R_1 = 3 \text{ k}\Omega$ and $R_2 = 6 \text{ k}\Omega$?



$$\begin{aligned} V_{\text{out}} &= R_2 / (R_1 + R_2) V_{\text{in}} \\ &= 6 \div (3 + 6) \times 9 \end{aligned}$$

Answer:

6 V

QUESTION 22

3 marks

If $R_2 = 5 \text{ k}\Omega$, what value of R_1 will produce an output voltage of 0.6 V? Give your answer in $\text{k}\Omega$.


Rearranging the voltage divider formula gives:

$$\begin{aligned} R_1 &= R_2 (V_{\text{in}} - V_{\text{out}}) / V_{\text{out}} \\ &= 5 \times (9 - 0.6) \div 0.6 \end{aligned}$$

Answer:

70 $\text{k}\Omega$

The diagram below represents the transfer characteristic for a voltage amplifier.

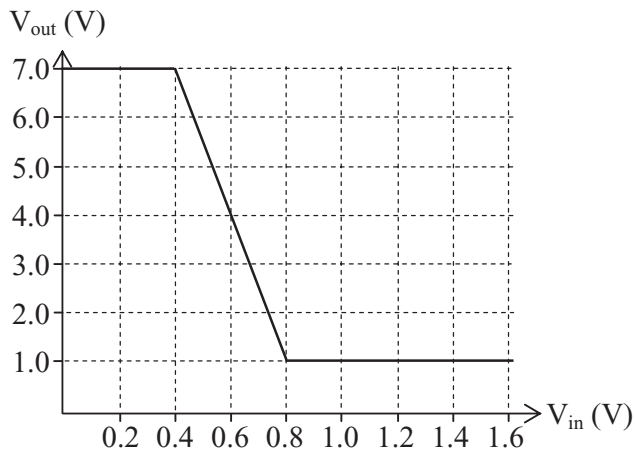

QUESTION 23

2 marks

State the input voltage that provides the ideal operating condition for this amplifier and the corresponding output voltage.

Answer:

input bias voltage = 0.6 V

output voltage = 4 V

The ideal operating condition is the centre of the sloping section of the transfer characteristic.

QUESTION 24

2 marks

Calculate the voltage gain of this amplifier.

$$\begin{aligned} \text{gain} &= \Delta V_{\text{out}} \div \Delta V_{\text{in}} \\ &= 6 \div 0.4 \\ &= 15 \end{aligned}$$

Answer:

15

QUESTION 25

1 mark

What is the value of V_{out} when $V_{\text{in}} = 0.7$ V?

Answer:

2.5 V

QUESTION 26

1 mark

What is the value of V_{out} when $V_{\text{in}} = 0.5$ V?

Answer:

5.5 V

QUESTION 27

2 marks

On the axes below, draw the output voltage for the following input voltage. Include values on the V_{out} axis.

